



# SYMBIOSIS INTERNATIONAL (DEEMED UNIVERSITY)

(Established under section 3 of the UGC Act, 1956)

Re-accredited by NAAC with 'A' grade (3.58/4) | Awarded Category – I by UGC

Seat No.						
----------	--	--	--	--	--	--

**Institute:** (0701) SYMBIOSIS INSTITUTE OF TECHNOLOGY, PUNE

**Programme:** (070122, 070124) BACHELOR OF TECHNOLOGY  
(COMPUTER SCIENCE, INFORMATION TECHNOLOGY)

**Batch:** 2015-19, 2016-20

**Semester:** III

**Course:** Digital Electronics and Logic Design

**Course Code:** 0701220305CS, 0701240305IT

**Date:** 12/6/2021

**Day :** Saturday

**Maximum Marks:** 60

**Time:** 3:00 to 5:30 pm

## Instructions:

1. All questions are compulsory.
2. Draw neat diagrams wherever necessary.
3. Use of non-programmable calculators is allowed.
4. Make suitable assumptions wherever required.

- Q.1 a)** Perform the following: 5 CO1
- i)  $(AF8)_{16} - (75)_{16} = ( )_{16}$  Hexadecimal subtraction using 16's complement.
- ii)  $(589)_{10} - (432)_{10} = ( )_{10}$  BCD subtraction using 10's complement.
- b)** What are the different universal gates? Explain any one universal gate with truth table. 5 CO1
- Q.2** Define any three characteristics of digital ICs. 6 CO2
- Q.3 a)** Design full adder using half adder along with truth table and K-map. 5 CO3
- b)** Simplify the Boolean function using K-map: 5 CO3
- $Y = \pi M(1, 2, 3, 5, 6, 7, 8, 10, 12, 13, 14, 15)$
- c)** Simplify the given expression using Boolean laws: 4 CO3
- $$Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}BC\bar{D}$$
- Q.4 a)** Explain Jk flip flop with preset and clear input. Also draw the truth table. 7 CO4
- What are the drawbacks of SR flip flop?



# SYMBIOSIS INTERNATIONAL (DEEMED UNIVERSITY)

(Established under section 3 of the UGC Act, 1956)

Re-accredited by NAAC with 'A' grade (3.58/4) | Awarded Category – I by UGC

Seat No.						
----------	--	--	--	--	--	--

- b) Describe 4-bit parallel in/serial out shift register (SISO). Show the waveform for serial output with the data input bits 1011 and clock shift/load. 7 C04
- c) Compare sequential and combinational circuits. 6 C04
- Q.5 Draw and explain ASM chart for mod 4 up counter with the condition that there exist an input signal W and if W=1, the count is incremented by 1 otherwise it remains same. 5 C05
- Q.6 Explain different components of PLA with diagram. 5 C06

\*\*\*\*\*