



# SYMBIOSIS INTERNATIONAL (DEEMED UNIVERSITY)

(Established under section 3 of the UGC Act, 1956)

Re-accredited by NAAC with 'A' grade (3.58/4) | Awarded Category – I by UGC

Seat No.						
----------	--	--	--	--	--	--

**Institute:** (0701) SYMBIOSIS INSTITUTE OF TECHNOLOGY, PUNE

**Programme:** (070122, 070124) BACHELOR OF TECHNOLOGY  
(COMPUTER SCIENCE, INFORMATION TECHNOLOGY)

**Batch:** 2017-21, 2018-22, 2019-23

**Semester:** III

**Course:** Digital Electronics and Logic Design

**Course Code:** 0701220305 CS, 0701240305 IT

**Date:** 12/6/2021

**Maximum Marks:** 45

**Day:** Saturday

**Time:** 3:00 to 4:30 pm

## Instructions:

1. All questions are compulsory.
2. Draw neat diagrams wherever necessary.
3. Use of non-programmable calculators is allowed.
4. Make suitable assumptions wherever required.

**Q.1 a)** Perform the following: 8 CO1

i)  $(B25)_{16} - (67)_{16} = ( )_{16}$  Hexadecimal subtraction using 16's complement.

ii)  $(456)_{10} - (542)_{10} = ( )_{10}$  BCD subtraction using 10's complement.

iii)  $(111110.1)_2 \div (0101)_2 = ( )_2$  Binary division.

iv)  $(636)_8 - (345)_8 = ( )_8$  Octal subtraction using 8's complement.

**Q.2 a)** Solve the following equation using algebraic simplification. Realize the answer using NOR gates only: 4 CO2

$$Y = A'B'C'D' + A'B'C'D + A'B'CD + A'B'CD'$$

**Q.3 a)** Solve the equation using k-map: 3 CO3

$$Y = \sum m(0, 1, 5, 9, 10, 13, 14) + d(3, 4, 7, 11, 15)$$

**b)** Convert the following expression into standard SOP form: 3 CO3

$$Y = AB + ABC' + BC'$$

**Q.4 a)** Design 1:8 demultiplexer using 1:4 demultiplexer circuits using truth table. 6 CO4

**b)** Design 4 bit binary to gray code convertor along with Truth table and K-map. 5 CO4



# SYMBIOSIS INTERNATIONAL (DEEMED UNIVERSITY)

(Established under section 3 of the UGC Act, 1956)

Re-accredited by NAAC with 'A' grade (3.58/4) | Awarded Category – I by UGC

Seat No.						
----------	--	--	--	--	--	--

- Q.5**
- a) Explain JK flip flop with preset and clear input. Also draw the truth table. **6 C05**  
What is the major drawback of JK flip flop?
- b) Draw and explain the circuit diagram of 4-bit Serial In/Parallel out (SISO) shift register. **6 C05**
- c) Compare sequential and combinational circuits. **4 C05**

\*\*\*\*\*